

# Operational Amplifier [Op-Amp]


## 5. OP-AMP APPLICATION (LOGARITHMIC / ANTI-LOGARITHMIC) ANSWER KEYS :

5.1	C	5.2	D	5.3	D	5.4	D	5.5	B
5.6	B								


## 6. OP-AMP APPLICATION (MULTIVIBRATOR / WAVEFORM GENERATOR) ANSWER KEYS :

6.1	B	6.2	C	6.3	C	6.4	A	6.5	C
6.6	B	6.7	D	6.8	A	6.9	A	6.10	C
6.11	0.635	6.12	0.8	6.13	A	6.14	A	6.15	0.798


### 6.6 Correction

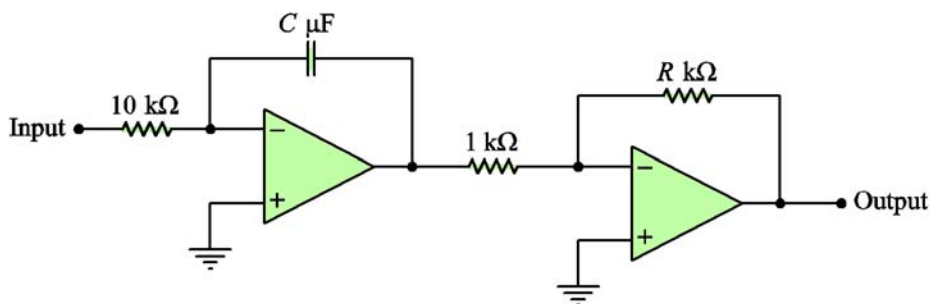

### 6.7 Correction option (D)

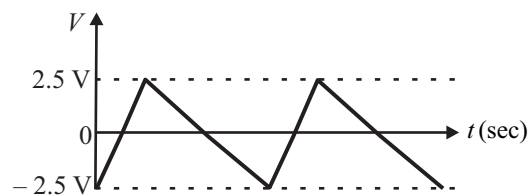

### 6.12 Correction

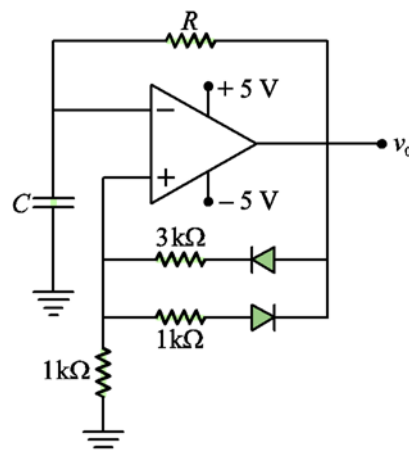


**7. OP-AMP APPLICATION (RECTIFIER / PEAK DETECTOR / CLIPPER / CLAMPER) ANSWER KEYS :**

7.1	B, C	7.2	*	7.3	B	7.4	D	7.5	D
7.6	D	7.7	B	7.8	A	7.9	B	7.10	D
7.11	C	7.12	1.6	7.13	A	7.14	B		

7.5 Op-Amp circuit shown in the given figure is

[IES EC 1995]

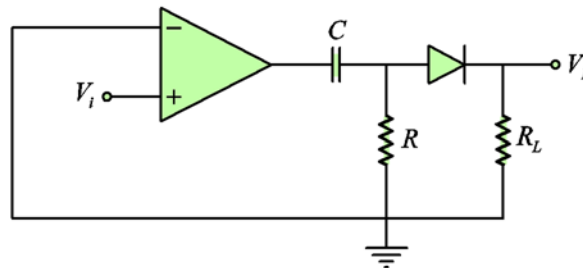


- (A) a sample and hold circuit
- (B) An integrator
- (C) A zero crossing detector
- (D) A half-wave precision rectifier

Ans. (D)

Sol. Modified circuit is shown below,


Assuming open loop gain  $A_{OL} = 10^6$

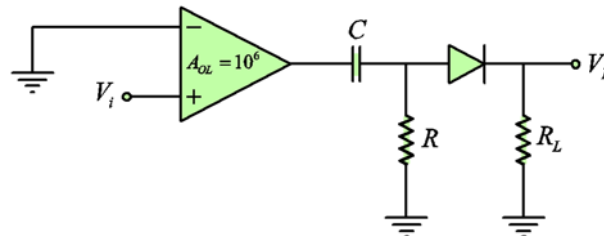

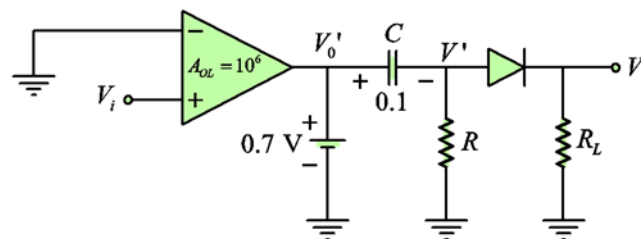1. For  $V_i > 0$ , ( $V_i = 0.7 \mu\text{V}$ )

$$V_0' = A_{OL} V_i$$


$$V_0' = 10^6 \times 0.7 \times 10^{-6} = 0.7 \text{ V}$$



Let capacitor charges with small voltage  $0.1 \text{ V}$ .

Applying KVL,  $-0.7 + 0.1 + V' = 0$
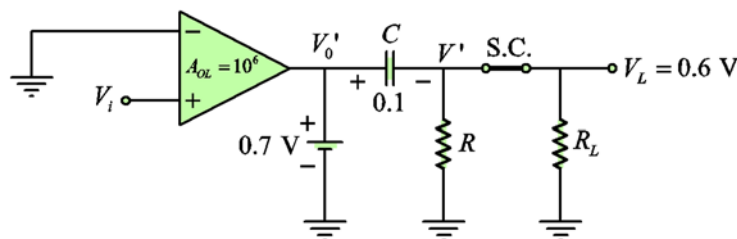
$$V' = 0.6 \text{ V} \Rightarrow \text{D is ON}$$




$$V_L \approx A_{OL} V_i \quad (\text{Capacitor takes some voltage})$$

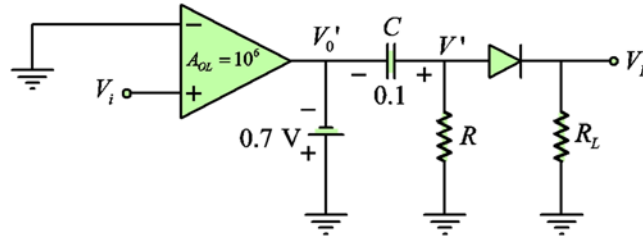2. For  $V_i < 0$ , ( $V_i = -0.7 \mu\text{V}$ )

$$V_0' = A_{OL} V_i$$


$$V_0' = 10^6 \times (-0.7 \times 10^{-6}) = -0.7 \text{ V}$$



Let capacitor charges with small voltage  $-0.1\text{ V}$ .

Applying KVL,  $0.7 - 0.1 + V' = 0$
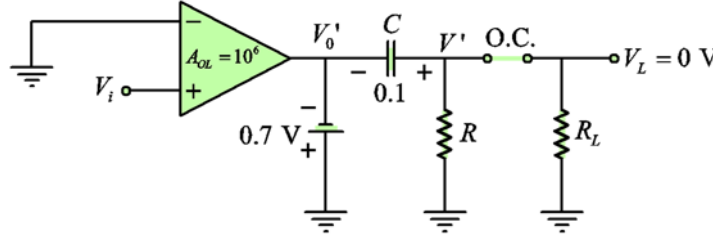
$$V' = -0.6\text{ V} \Rightarrow D \text{ is OFF}$$









$$V_L = 0\text{ V}$$

In positive half cycle  $V_L = A_{ol}V_i$

In negative half cycle  $V_L = 0$


Hence it is a half wave rectifier circuit. Since for small value of input ( $0.7\text{ }\mu\text{V}$ ) we get output. Hence it is a precision half wave rectifier circuit.

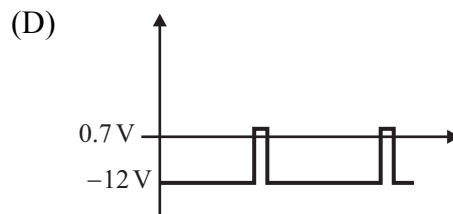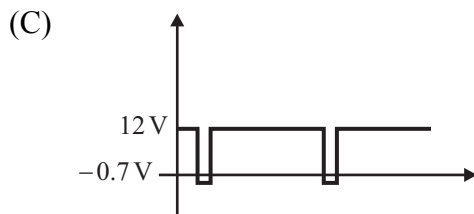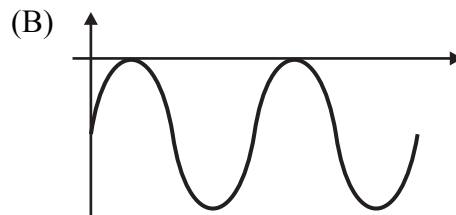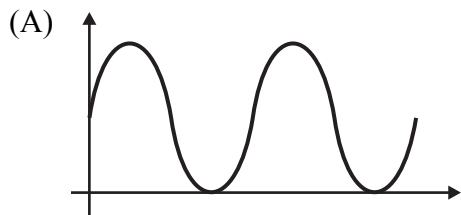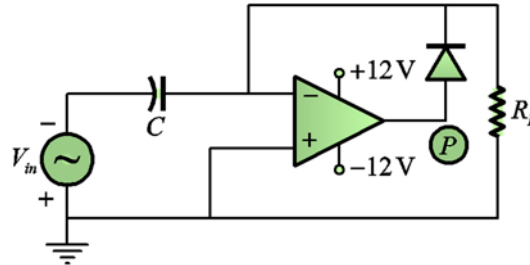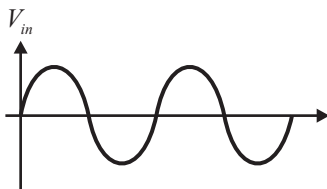**7.6** For a given sinusoidal input voltage, the voltage waveform at point P of the clamper circuit shown in figure will be [GATE EE 2006, IIT-Kharagpur]





**Ans. (D)**

**Sol. Case I :** During negative half cycle of input, output of *op-amp*  $V_0 = +V_{sat}$  and diode *D* is forward biased.


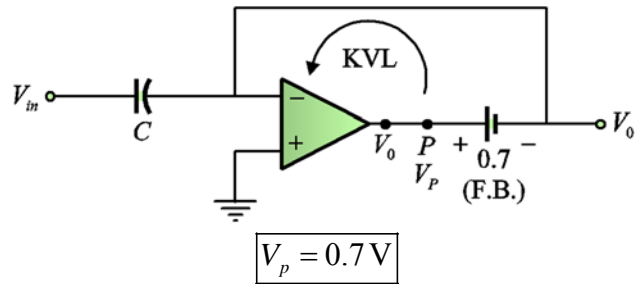


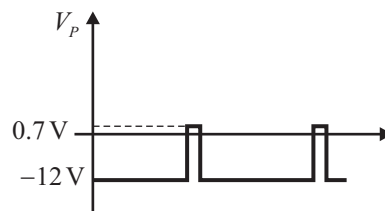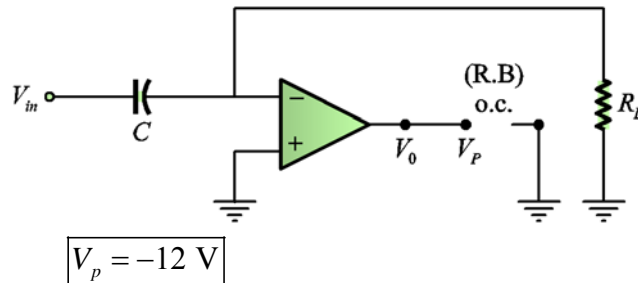**Case II :** During positive half cycle of input, output of op-amp  $V_o = -V_{sat}$  and diode is reversed biased



Hence the correct option is (D).

If position of P is changed

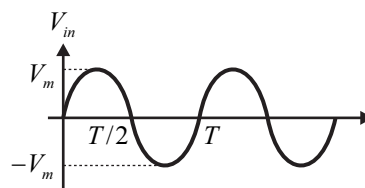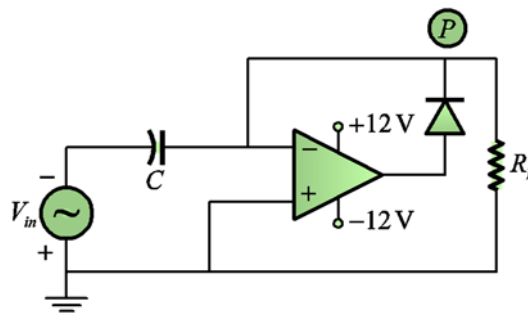

For positive half cycle

At  $t = \frac{T}{4}$ ,  $V_{in} = V_m$

Then  $NI > I$

So  $V_o = +V_{sat}$ , diode is ON

Capacitor will charge up to  $V_C = V_{sat} - (-V_m) = V_{sat} + V_m$

And capacitor will hold this voltage due to high value of load resistance

At  $t = \frac{3T}{4}$

$$V_p = V_{sat} + 2V_m$$

In the next negative half cycle  $V_p$  will discharge up to  $+V_{sat}$

So diode is OFF


Applying KVL in the loop shown

$$+V_{in} - (V_{sat} + V_m) + V_p = 0$$

$$V_p = V_{sat} + V_m - V_{in}$$

In this case circuit behaves as a positive clamper.

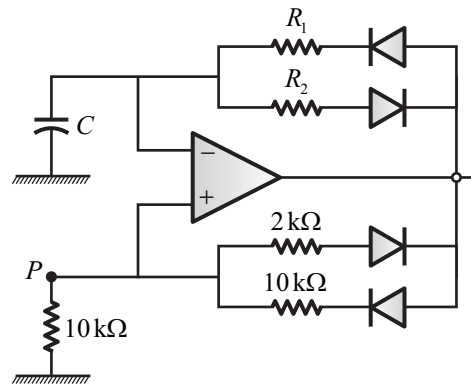
7.8 A relaxation oscillator is made using Op-Amp as shown in below figure. The supply voltages of the Op-Amp are  $\pm 12\text{ V}$ . The voltage waveform at point P will be [GATE EE 2006, IIT-Kharagpur]



- (A)
- (B)
- (C)
- (D)

Ans. (C)

Sol. Given : A relaxation oscillator

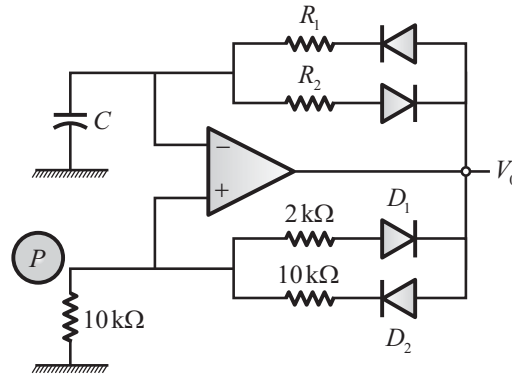

Output voltage of relaxation oscillator mode using *op*-amp will switch + 12 V and – 12 V  
 When  $V_0 = +12\text{ V}$ , diode  $D_2$  will be forward biased

$$\therefore V_p = +12 \times \frac{10}{10+10}$$


$$\therefore \boxed{V_p = +6\text{ V}}$$

when  $V_0 = -12\text{ V}$ , diode  $D_1$  will be forward biased

$$V_p = -12 \times \frac{10}{10+2}$$

$$\therefore \boxed{V_p = -10\text{ V}}$$

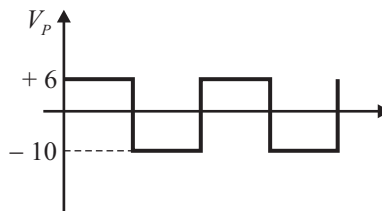Therefore the voltage waveform at point  $P$




**8. OP-AMP CHARACTERISTICS (SLEW RATE) ANSWER KEYS :**

8.1	D	8.2	C	8.3	159	8.4	B	8.5	C
8.6	A	8.7	B	8.8	C	8.9	A	8.10	D
8.11	A	8.12	B	8.13	D	8.14	C	8.15	B
8.16	D	8.17	B						

**9. OP-AMP CHARACTERISTICS (CMRR) ANSWER KEYS :**

9.1	C	9.2	A	9.3	$V_{cm} = V_0$	9.4	140	9.5	D
9.6	D	9.7	C	9.8	B	9.9	D	9.10	A
9.11	B	9.12	A	9.13	C	9.14	D	9.15	40.4

**9.5 Correction**

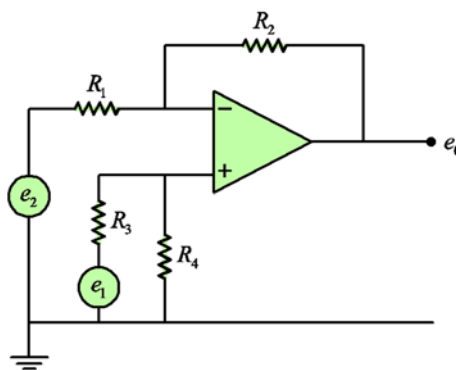


**10. OP-AMP CHARACTERISTICS (BIAS / OFFSET) ANSWER KEYS :**

10.1	C	10.2	D	10.3	D	10.4	B	10.5	D
10.6	C	10.7	D	10.8	A	10.9	C	10.10	C
10.11	C	10.12	D	10.13	C	10.14	D	10.15	413.8
10.16	20								

**10.1** An op amp has an offset voltage of 1 mV and is ideal in all other respects. If this op amp is used in the circuit shown in the given figure, the output voltage will be (select the nearest value).


[GATE EC 1992, IIT-Delhi]

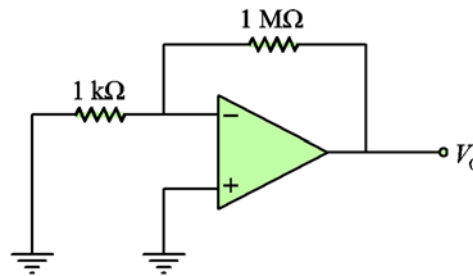

- (A) 1 mV                      (B) 1 V                      (C)  $\pm 1$  V                      (D) 0 V

Ans. (C)

Sol.

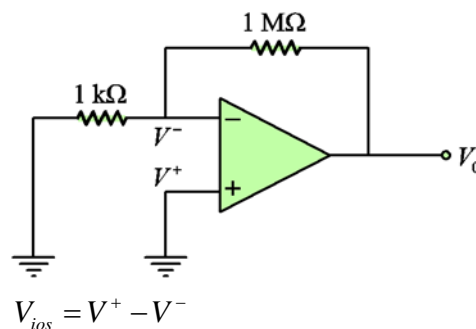

If  $V^+ = 1$  mV and  $V^- = 0$

$$\Rightarrow V_{ios} = 1 \text{ mV}$$

$$V_o = \left[ 1 + \frac{R_f}{R} \right] V_{ios}$$

$$V_o = \left[ 1 + \frac{10^3}{1} \right] 1 = 1 \text{ V}$$

If  $V^- = 1$  mV and  $V^+ = 0$

$$\Rightarrow V_{ios} = -1 \text{ mV}$$

$$V_o = \left[ 1 + \frac{R_f}{R} \right] V_{ios}$$


$$V_o = \left[ 1 + \frac{10^3}{1} \right] (-1) = -1 \text{ V}$$

So  $V_o = \pm 1$  V

**Key point :**

If option has + 1 and - 1 V then we will prefer + 1 V.

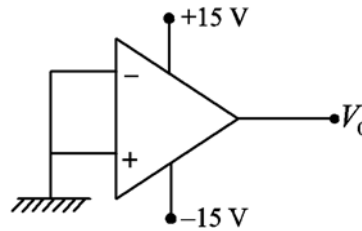- 10.6** If the Op-Amp in given figure, has an input offset voltage of 5 mV and an open-loop voltage gain of 10,000, then  $V_0$  will be [GATE EC 2000, IIT-Kharagpur]



- (A) 0 V (B) 5 mV  
(C) +15 V or -15 V (D) +50 V or -50 V

**Ans. (C)**

**Sol.**  $V_{OOS} = A_{ios} \times A_{OL}$

$$V_{OOS} = 5 \times 10^{-3} \times 10^4 = 50 \text{ V (saturated)}$$

$$V_{OOS} = \pm 15 \text{ V}$$

### 11. OP-AMP APPLICATION (INSTRUMENTATION AMPLIFIER) :

11.1	B	11.2	D	11.3	C	11.4	A	11.5	A
------	---	------	---	------	---	------	---	------	---

### 12. OP-AMP APPLICATION (SAMPLE AND HOLD CIRCUIT) ANSWER KEYS :

12.1	$5 \times 10^{-3}$	12.2	B	12.3	C	12.4	D	12.5	B
12.6	B								

### 13. OP-AMP APPLICATION (REGULATOR) ANSWER KEYS :

13.1	C	13.2	C	13.3	D	13.4	B	13.5	C
13.6	$\frac{1092}{1094}$	13.7	2.8	13.8	1.145				

### 14. DIFFERENTIAL AMPLIFIER ANSWER KEYS :


14.1	B	14.2	B	14.3	A	14.4	A	14.5	C
14.6	A	14.7	B	14.8	A	14.9	B	14.10	D
14.11	A	14.12	C	14.13	A	14.14	B	14.15	B
14.16	1.5								

### 15. MISCELLANEOUS ANSWER KEYS :

15.1	A	15.2	B	15.3	A	15.4	B	15.5	C
15.6	D	15.7	A	15.8	D	15.9	A	15.10	B
15.11	C	15.12	D	15.13	D	15.14	D	15.15	A
15.16	A	15.17	A	15.18	C	15.19	B	15.20	D
15.21	A	15.22	D	15.23	D	15.24	B	15.25	D
15.26	D	15.27	B	15.28	C	15.29	B	15.30	C
15.31	D	15.32	B	15.33	D	15.34	B	15.35	C
15.36	D	15.37	B	15.38	A	15.39	C	15.40	D
15.41	B	15.42	B	15.43	3	15.44	800	15.45	C
15.46	C								



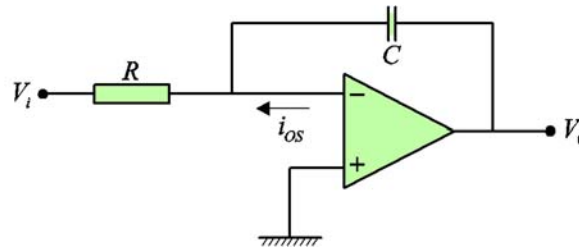**15.13** An integrator circuit is shown in below figure. The Op-Amp is of type 741 and has an input offset current  $i_{os}$  of  $1 \mu\text{A}$ .  $C$  is  $1 \mu\text{F}$  and  $R$  is  $1 \text{ M}\Omega$ . If the input  $V_i$  is a  $1 \text{ kHz}$  square wave of  $1 \text{ V}$  peak to peak, the output  $V_o$ , under steady state condition, will be [GATE IN 2003, IIT-Madras]




- (A) a square wave of  $1 \text{ V}$  peak to peak  
 (B) a triangular wave of  $1 \text{ V}$  peak to peak  
 (C) positive supply voltage  $+V_{CC}$   
 (D) negative supply voltage  $-V_{CC}$

**Ans. (D)**

**Sol.** By Super position theorem

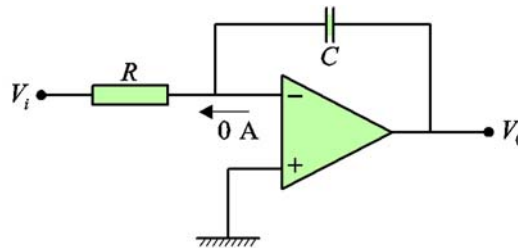1. Consider voltage source  $V_i$ , ( $i_{os} = 0$ )




Time constant,  $\tau = RC = 10^6 \times 10^{-6} = 1 \text{ sec}$

$V_i$  is a  $1 \text{ kHz}$  square wave of  $1 \text{ V}$  peak to peak. So time period  $T = \frac{1}{f} = \frac{1}{1 \text{ kHz}} = 1 \text{ msec}$

Input changes very quickly so capacitor does not have enough time to charge or discharge.

So  $V_C = 0 \Rightarrow V_o = 0 \text{ V}$

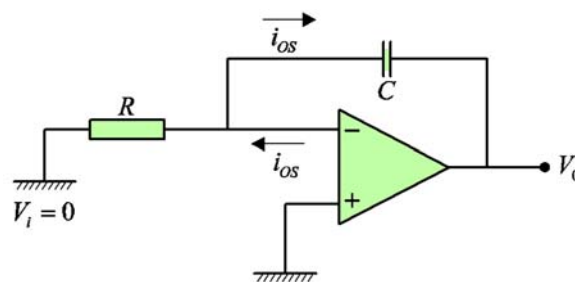2. Consider only  $i_{os}$ , ( $V_i = 0$ )



$$i_{os} = C \frac{d}{dt} (0 - V_o)$$


$$i_{os} = -C \frac{d}{dt} V_o$$

$$V_o = -\frac{1}{C} \int i_{os} dt$$

$$V_o = \frac{-10^{-6}}{10^{-6}} \int dt$$

$$[C = 1 \mu\text{F}, i_{os} = 1 \mu\text{A}]$$


$$V_o = -t$$

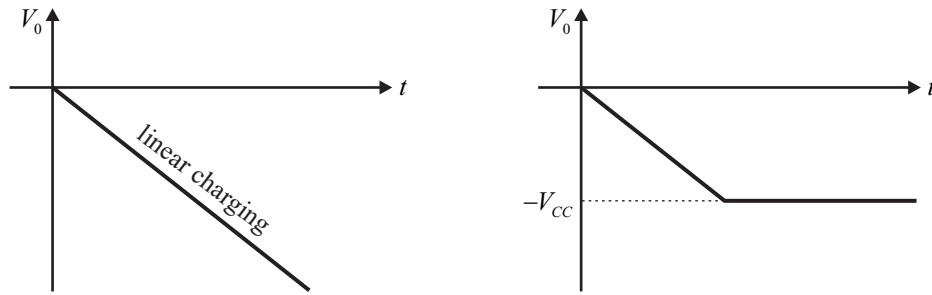

Output of Op-Amp lies between  $+V_{CC}$  and  $-V_{CC}$ . So  $V_o$  saturate at  $-V_{CC}$ .

15.18 Consider the following circuit

[IES EC 2004]

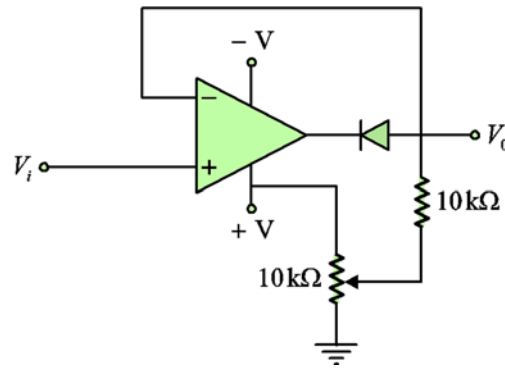


How does the below circuit work?

- (A) As a logarithmic amplifier
- (C) As a positive clipper

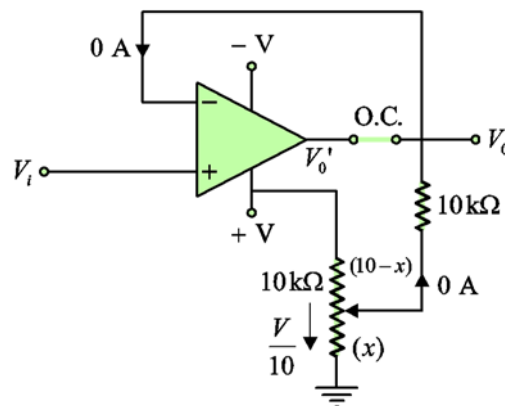- (B) As a negative clipper
- (D) As a half-wave rectifier


Ans. (C)

Sol. For  $V_i > 0$ ,  $V_o' = +V \Rightarrow D$  is OFF




From figure  $V_o = \frac{xV}{10}$  (constant)

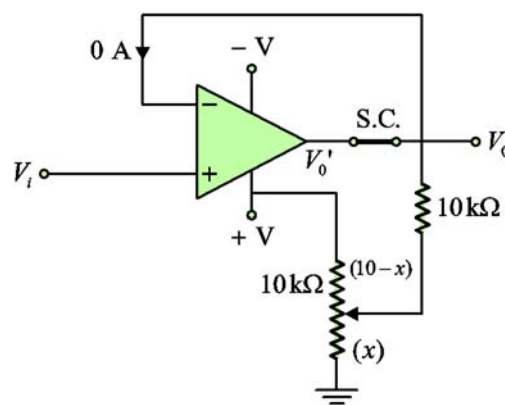For  $V_i < 0$ ,  $V_o' = -V \Rightarrow D$  is ON




Voltage follower circuit  $V_o = V_i$ .

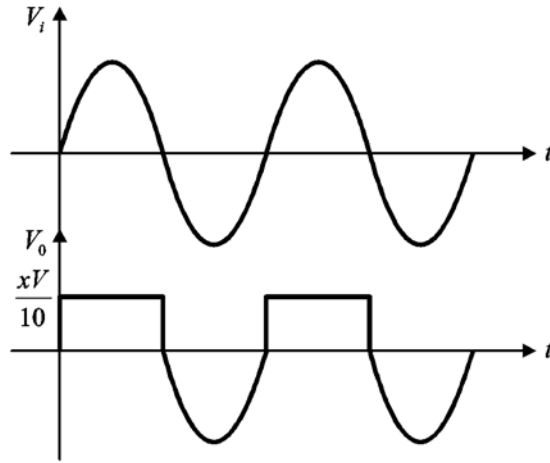

Since maximum positive portion at output gets clipped hence the circuit is clipper circuit.

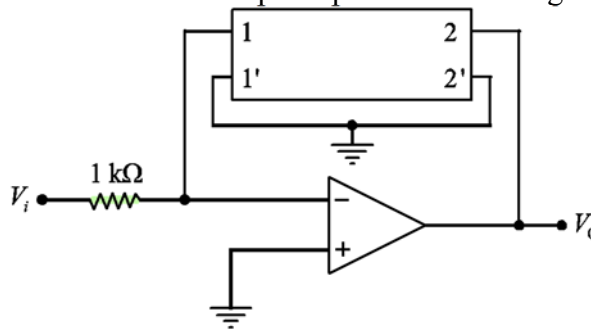
15.26 Consider the linear circuit with an ideal Op-Amp shown in the figure below.



The Z-parameters of the two port feedback network are  $Z_{11} = Z_{22} = 11 \text{ k}\Omega$  and  $Z_{12} = Z_{21} = 1 \text{ k}\Omega$   
 The gain of the amplifier is [GATE IN 2007, IIT-Kanpur]

- (A) + 110
- (B) + 11
- (C) - 1
- (D) - 120

Ans. (D)  
 Sol.

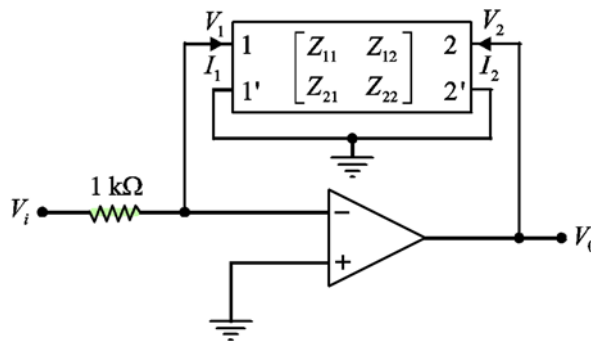

Given : Z-parameter =  $\begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix} = \begin{bmatrix} 11 & 1 \\ 1 & 11 \end{bmatrix}$  ..... (i)

Standard Z-parameter equation is given by,

$$V_1 = Z_{11}I_1 + Z_{12}I_2$$

$$V_2 = Z_{21}I_1 + Z_{22}I_2$$

So, from equation (i),

$$V_1 = 11I_1 + I_2 \quad \text{..... (ii)}$$

$$V_2 = I_1 + 11I_2 \quad \text{..... (iii)}$$

$$V_1 = 0 \quad \text{[From VGC]}$$

From equation (ii),

$$11I_1 + I_2 = 0$$

$$I_2 = -11I_1 \quad \text{..... (iv)}$$

$$V_0 = V_2 \quad \text{[From figure]}$$

From equation (iii),

$$V_0 = I_1 + 11I_2$$

$$V_0 = I_1 + 11(-11I_1)$$

[From equation (iv)]

$$V_0 = -120I_1$$


Applying KCL at inverting terminal

$$I_1 = \frac{V_i}{1} \Rightarrow V_i = I_1$$

So,  $V_0 = -120V_i$

$$\text{Gain} = \frac{V_0}{V_i} = -120$$

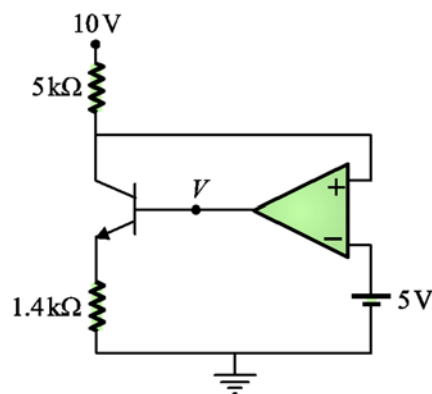
- 15.31** In the circuit shown below, the Op-Amp is ideal, the transistor has  $V_{BE} = 0.6 \text{ V}$  and  $\beta = 150$ . Decide whether the feedback in the circuit is positive or negative and determine the voltage  $V$  at the output of the Op-Amp. [GATE EC 2009, IIT-Roorkee]



- (A) Positive feedback,  $V = 10 \text{ V}$   
 (C) Negative feedback,  $V = 5 \text{ V}$

- (B) Positive feedback,  $V = 0 \text{ V}$   
 (D) Negative feedback,  $V = 2 \text{ V}$

**Ans. (D)**  
**Sol.**

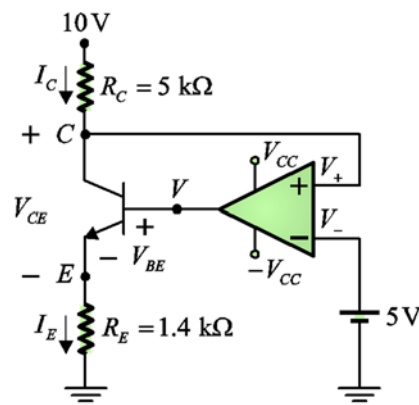

Let us first assume that there is a positive feedback. Then  $V$  can either  $+V_{CC}$  or  $-V_{CC}$ .

Let  $V_{CC} = 10 \text{ V}$

Now, for there to be a feedback, transistor must be ON.

$V$  can not be  $-V_{CC}$

$$V = +V_{CC} = +10 \text{ V}$$

Applying KVL in emitter loop :

$$V - V_{BE} - I_E R_E = 0$$

$$I_E = \frac{10 - 0.6}{1.4} = 6.7 \text{ mA}$$

$$I_C \approx I_E = 6.7 \text{ mA} \quad [\beta \text{ is large}]$$

$$V_C = 10 - I_C R_C = 10 - 6.7 \times 5$$

$$V_C = -23.5 \text{ V}$$

$$V_E = I_E R_E = 9.6 \text{ V}$$

$V_{CE} < 0$  or CB junction is forward biased

The transistor is in saturation region.

$$V_{CE} = V_{CE, sat} = 0.2 \text{ V} \quad [\text{say}]$$

$$10 - I_C R_C - V_{CE} - I_E R_E = 0$$

$$\text{So, } I_C \approx I_E = \frac{10 - 0.2}{R_C + R_E} = \frac{9.8}{5 + 1.4}$$

$$I_C \approx I_E = 1.53 \text{ mA}$$

$$V_C = 10 - I_C R_C$$

$$V_C = 10 - 1.53 \times 5 = 2.65 \text{ V}$$

$$V_+ = V_C = 2.65 \text{ V}$$

But  $V_- = 5 \text{ V}$

$$V_+ < V_-$$

$$V = -V_{CC}$$

But we assumed that  $V = +V_{CC}$

Hence there can't be positive feedback.

Therefore Op-Amp will be in negative feedback.

Then  $V_+ = V_- = 5 \text{ V}$  [From VGC]

$$V_C = +5 \text{ V}$$

$$I_C = \frac{10 - V_C}{R_C} = \frac{10 - 5}{5} = 1 \text{ mA}$$

$$I_E \approx I_C = 1 \text{ mA}$$


$$V = V_{BE} + I_E R_E$$

$$V = 0.6 + 1 \times 1.4 = 2 \text{ V}$$

Hence, there will be a negative feedback with  $V = 2 \text{ V}$ .

- 15.36** The transfer characteristic of the circuit drawn below is observed on an oscilloscope used in XY mode. The display on the oscilloscope is shown on the right hand side.  $V_i$  is connected to the X input with a setting of 0.5 V/div, and  $V_o$  is connected to the Y input with a setting of 2 V/div. The beam is positioned at the origin when  $V_i$  is zero.

[GATE IN 2011, IIT-Madras]

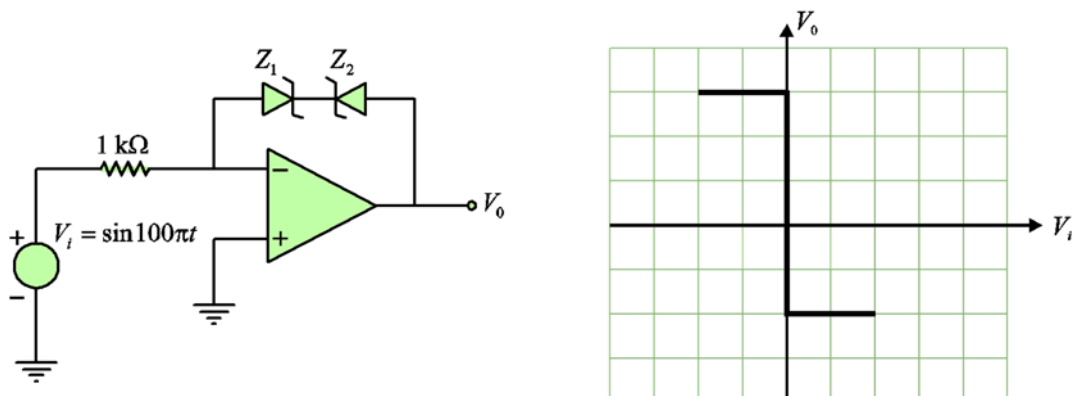

Assuming that the Op-Amp is ideal and the zener diodes have forward biased voltage drop of 0.7 V, the values of reverse break-down voltages of  $Z_1$  and  $Z_2$  are, respectively,

(A) 3.3 V and 5.3 V


(B) 4.7 V and 6.7 V

(C) 6.7 V and 4.7 V

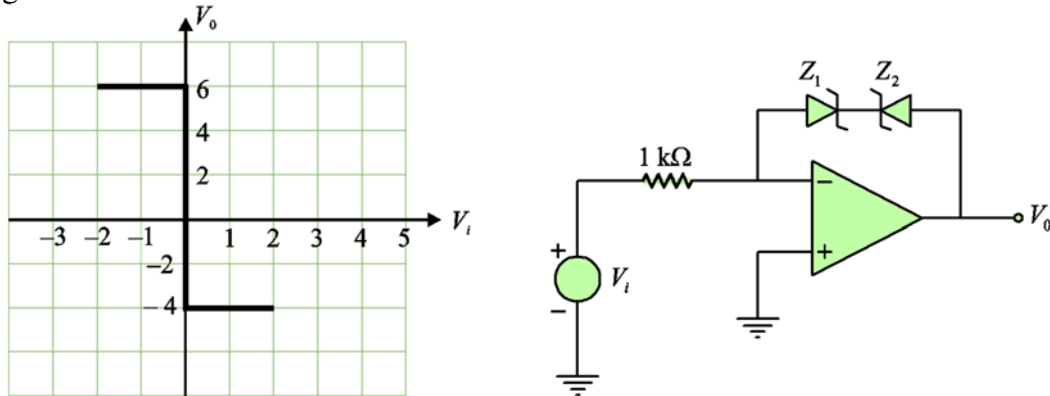(D) 5.3 V and 3.3 V


Ans. (D)

Sol.  $V_i$  is connected to the X input with a setting of 0.5 V/div, and  $V_o$  is connected to the Y input with a setting of 2 V/div. So the transfer characteristics can be modified as



When  $V_i$  is +ve then  $Z_1$  is F.B. and  $Z_2$  is R.B. so replace  $Z_1$  by forward voltage drop.

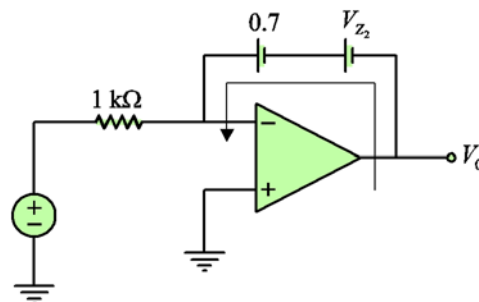When  $V_i$  is +ve, then  $V_{out} = -4$  Volts (from graph)



Applying KVL in the loop shown

$$-V_o - V_{Z_2} - 0.7 = 0$$


$$V_o = -V_{Z_2} - 0.7$$

$$-4 = -V_{Z_2} - 0.7$$

$$V_{Z_2} = 3.3 \text{ V}$$

When  $V_i$  is -ve then  $Z_1$  is RB and  $Z_2$  is FB.

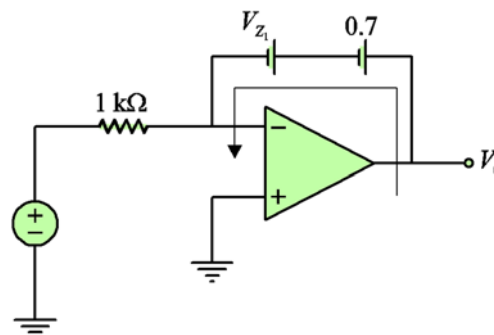So replace  $Z_2$  by forward voltage drop and when  $V_i = -ve$   $V_{out} = 6$  volts (From graph)



Applying KVL in the loop shown


$$-V_o + V_{Z_1} + 0.7 = 0$$

$$V_o = 0.7 + V_{Z_1}$$

$$6 = 0.7 + V_{Z_1}$$

$$V_{Z_1} = 5.3 \text{ V}$$

## 15.42 Correction

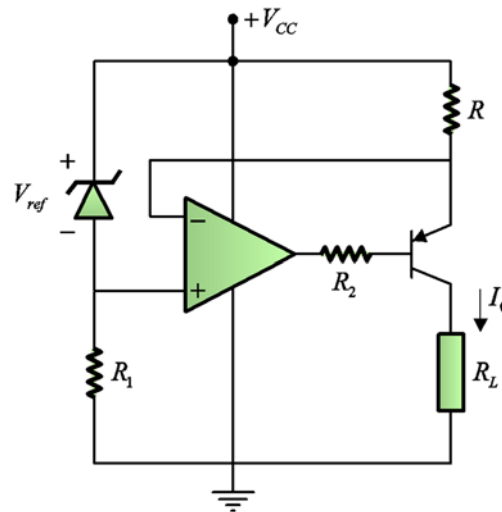

15.45 The transient response rise time (unity gain) of an Op-Amp is  $0.05 \mu\text{s}$ . The small signal bandwidth is [IES EC 2016]

- (A) 7 kHz                      (B) 20 kHz                      (C) 7 MHz                      (D) 20 MHz

Ans. (C)

Sol. Rise time in terms of bandwidth is given by,

$$t_r = \frac{0.35}{\text{B.W.}}$$

$$\text{Bandwidth} = \frac{0.35}{t_r} = \frac{0.35}{0.05 \mu\text{s}} = \frac{35}{5} \times 10^6 \text{ Hz} = 7 \text{ MHz}$$

## PRACTICE TEST - 01 ANSWER KEYS :

1.	1.5	2.	C	3.	210	4.	B	5.	B
6.	40	7.	D	8.	-11	9.	245	10.	8
11.	C	12.	2	13.	6	14.	-5	15.	610
16.	-5	17.	-1	18.	B	19.	A	20.	A
21.	2	22.	C	23.	A	24.	6	25.	D

## PRACTICE TEST - 02 ANSWER KEYS :

1.	-2.5	2.	D	3.	A	4.	C	5.	B
6.	A	7.	D	8.	A	9.	C	10.	B
11.	B	12.	B	13.	B	14.	2.4	15.	C
16.	C	17.	C	18.	B	19.	D	20.	C
21.	B	22.	C	23.	B	24.	A	25.	A
26.	C	27.	D	28.	B	29.	A	30.	37.78

